

Chua Circuit Equations

Choose as the dynamical variables:

- V_1 : the voltage across capacitor C_1 (and the nonlinear resistance)
- V_2 : the voltage across capacitor C_2 (and the voltage across the inductor)
- I : the current through the inductor.

Kirchoff's laws then give

$$\begin{aligned} C_1 \frac{dV_1}{dt} &= R^{-1} (V_2 - V_1) - g(V_1) \\ C_2 \frac{dV_2}{dt} &= -R^{-1} (V_2 - V_1) + I \\ L \frac{dI}{dt} &= -rI - V_2 \end{aligned}$$

where $g(V)$ is the conductance (I/V) for the effective nonlinear resistance (and is a negative quantity for the circuit). If we scale resistances by R_1 , times by $C_1 R_1$, measure voltages with respect to the switch point V_c in $g(V)$, and currents with respect to V_c/R_1 , we get the equations

$$\begin{aligned} \frac{dX}{dt} &= a(Y - X) - \bar{g}(X) \\ \frac{dY}{dt} &= \sigma[-a(Y - X) + Z] \\ \frac{dZ}{dt} &= -c(Y + \bar{r}Z) \end{aligned}$$

with $X = V_1/V_c$, $Y = V_2/V_c$, $Z = R_1 I/V_c$, and then the parameters of the equations are:

| | | |
|-----------|---------------|-------|
| a | R_1/R | 0.923 |
| b | $1 - R_1/R_2$ | 0.636 |
| c | $C_1 R_1^2/L$ | 0.779 |
| σ | C_1/C_2 | 0.066 |
| \bar{r} | r/R_1 | 0.071 |

with the third column giving the values for the initial parameters of the applet. The nonlinear conductance is

$$\bar{g}(X) = \begin{cases} -X & |X| < 1 \\ [-1 + b(|X| - 1)] \operatorname{sgn}(X) & 1 < |X| < 10 \\ [10(|X| - 10) + (9b - 1)] \operatorname{sgn}(X) & |X| > 10 \end{cases}$$

where the expression for $|X| > 10$ is needed for stability, and corresponds to complicated saturation effects in the actual circuit. Note that the slope is -1 for $|X| < 1$, $-b$ for $1 < |X| < 10$, and 10 for $|X| > 10$.

The time independent solutions are at

$$X = \pm \frac{1-b}{\frac{a}{1+\bar{r}a} - b} \simeq \pm \frac{1-b}{a-b}, \quad Y = \frac{a\bar{r}}{1+\bar{r}a} X \simeq 0, \quad Z = -\frac{a}{1+\bar{r}a} X \simeq -aX.$$

Linearizing about the fixed points gives solutions varying as $e^{\lambda t}$ with λ given by the eigenvalues of the stability matrix

$$\begin{bmatrix} -a+b & a & 0 \\ \sigma a & -\sigma a & \sigma \\ 0 & -c & -\bar{r}c \end{bmatrix}$$

and positive λ means the stationary solutions are unstable.

Some examples of the eigenvalues λ_1 , λ_2 , and λ_3 :

| a | b | c | σ | \bar{r} | λ_1 | $\lambda_{2,3}$ |
|-------|-------|-------|----------|-----------|-------------|--------------------------------------|
| 0.923 | 0.636 | 0.779 | 0.066 | 0.071 | -.40191 | $-6.5991 \times 10^{-4} \pm .17715i$ |
| 1 | 0.636 | 0.779 | 0.066 | 0.071 | -.48631 | $5.0174 \times 10^{-4} \pm .1836i$ |
| 0.923 | 0.636 | 0.779 | 0.066 | 0 | -.40617 | $2.9125 \times 10^{-2} \pm .18836i$ |
| 1 | 0.636 | 0.779 | 0.066 | 0 | -.48897 | $2.9486 \times 10^{-2} \pm .1934i$ |

In each case there is one decaying (negative) eigenvalue, and a pair of oscillating (complex) eigenvalues, with an imaginary part around 0.2, corresponding roughly to the $1/\sqrt{LC_2}$ oscillation frequency, and a real part that is either slightly negative (decaying oscillation) as for the parameters of the applet (first row) or slightly positive (growing oscillation) for the other rows.